

Computing in/using memory -- II

Asif Ali Khan

Fall Semester 2024




Department of Computer Systems Engineering

UET Peshawar, Pakistan


Nov 28, 2024

Recap: Compute-in-memory (CIM)

   
- ❑ The CIM paradigm aims to completely eliminate the data movement
- ❑ The fundamental idea is to exploit the physical properties of the memory devices to perform computations
- ❑ Not every computation can be performed with every technology



 
Recap: Emerging nonvolatile memories (NVMs)




Zhang et al., 2020

 

G. Yu, 2020

 


Lim et al, 2015

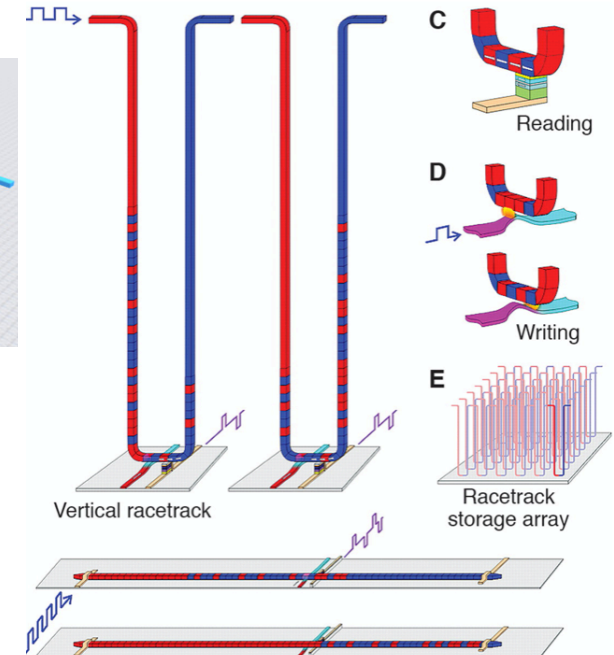

Parkin et al, 2008

- ❑ Other options: FeFET, FeRAM etc
- ❑ Each technology has its strengths and challenges
- ❑ PCM and MRAM receive a lot of traction in industry


Recap: CIM crossbar

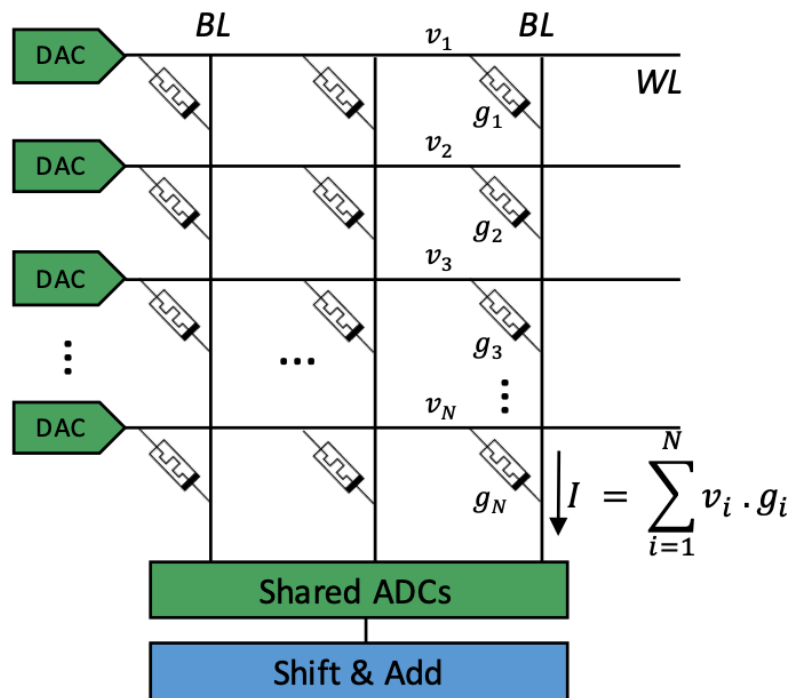


- ❑ Program one operand into memristors devices (conductance)
- ❑ Enable all wordlines simultaneously and apply another operand as input
- ❑ The accumulated current at the bitlines using Kirchoff's law produces the outcome of dot product
- ❑ Analog domain computation – results are approximate

CIM logic

 - ❑ Performs bulk-bitwise logic operations in-memory (operands and output are stored in the same array)




CIM logic

 


- ❑ Performs bulk-bitwise logic operations in-memory (operands and output are stored in the same array)
- ❑ Have applications in cryptography, databases and other domains

CIM logic

 


- ❑ Performs bulk-bitwise logic operations in-memory (operands and output are stored in the same array)
- ❑ Have applications in cryptography, databases and other domains
- ❑ The fundamental idea is still current/charge sharing

CIM logic

 


- ❑ Performs bulk-bitwise logic operations in-memory (operands and output are stored in the same array)
- ❑ Have applications in cryptography, databases and other domains
- ❑ The fundamental idea is still current/charge sharing
- ❑ The exact implementation depends on the specific technology

CIM-logic using DRAM

 


CIM-logic using DRAM

 

Before discussing CIM-DRAM, let's first look at RowClone


CIM-logic using DRAM

 

❑ Before discussing CIM-DRAM, let's first look at RowClone


If a DRAM cell is connected to a bitline that is at a stable state (either V_{DD} or 0) instead of the equilibrium state ($\frac{1}{2}V_{DD}$), then the data in the cell is overwritten with the data (voltage level) on the bitline.

CIM-logic using DRAM

 


❑ To RowClone **src** to **dst**, ACTIVATE-ACTIVATE-PRECHARGE (AAP) is needed:

CIM-logic using DRAM

 


- ❑ To RowClone **src** to **dst**, ACTIVATE-ACTIVATE-PRECHARGE (AAP) is needed:
 - ❑ ACTIVATE **src**, the data appears on the bitlines (senseamps)

CIM-logic using DRAM

 

- ❑ To RowClone **src** to **dst**, ACTIVATE-ACTIVATE-PRECHARGE (AAP) is needed:
 - ❑ ACTIVATE **src**, the data appears on the bitlines (senseamps)
 - ❑ ACTIVATE **dst**, the stable bitline contents replaces contents of the **dst** row

CIM-logic using DRAM

 


- ❑ To RowClone **src** to **dst**, ACTIVATE-ACTIVATE-PRECHARGE (AAP) is needed:
 - ❑ ACTIVATE **src**, the data appears on the bitlines (senseamps)
 - ❑ ACTIVATE **dst**, the stable bitline contents replaces contents of the **dst** row
 - ❑ A PRECHARGE command brings the bitline to the equilibrium state ($V_{DD}/2$)

CIM-logic using DRAM

- ❑ Simultaneous activation of three rows in a DRAM array results in bit-wise majority
 - ❑ At least two cells have to be 1, for the output to be 1
 - ❑ The operation is called *triple row activation* (TRA)

CIM-logic using DRAM

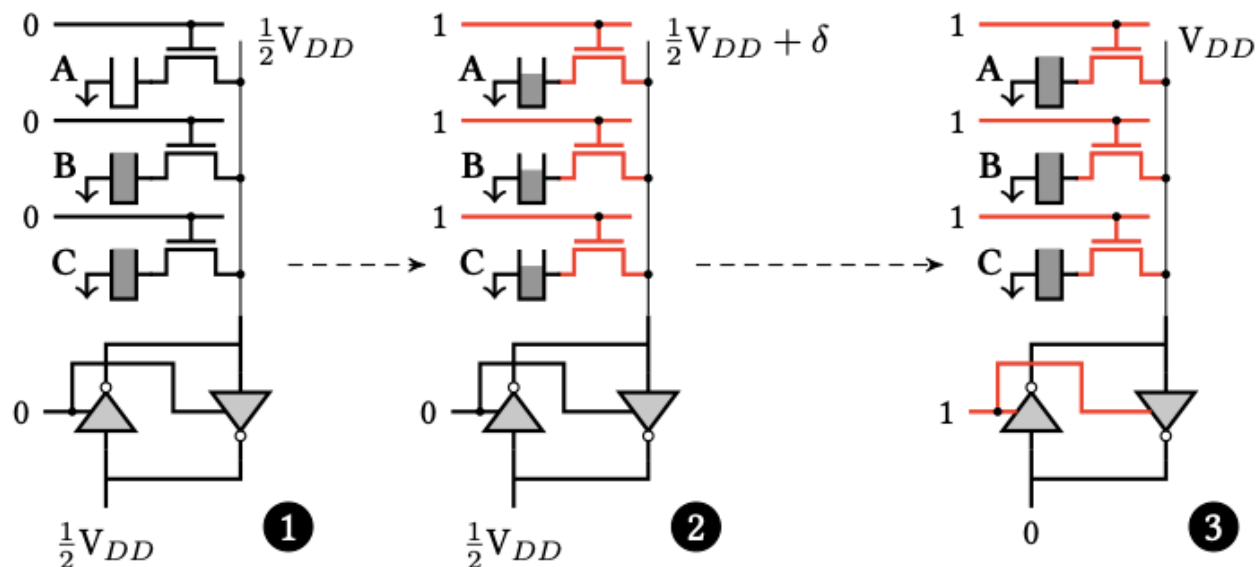- ❑ Simultaneous activation of three rows in a DRAM array results in bit-wise majority
 - ❑ At least two cells have to be one, for the output to be one
 - ❑ The operation is called *triple row activation* (TRA)



CIM-logic using DRAM

- ❑ Lets say A , B , C represent the state of the three cells
- ❑ The final state of the bitline is: $AB + AC + BC$

CIM-logic using DRAM

- ❑ Lets say A , B , C represent the state of the three cells
- ❑ The final state of the bitline is: $AB + AC + BC$
- ❑ This can be rewritten as: $C \cdot (A+B) + C' \cdot (AB)$


CIM-logic using DRAM

- ❑ Lets say A , B , C represent the state of the three cells
- ❑ The final state of the bitline is: $AB + AC + BC$
- ❑ This can be rewritten as: $C \cdot (A+B) + C' \cdot (AB)$
- ❑ By controlling C , we can implement both AND and OR operations
 - ❑ $C=1$, to implement OR and $C=0$, to implement AND operation

CIM-logic using DRAM


- ❑ Lets say A , B , C represent the state of the three cells
- ❑ The final state of the bitline is: $AB + AC + BC$
- ❑ This can be rewritten as: $C \cdot (A+B) + C' \cdot (AB)$
- ❑ By controlling C , we can implement both AND and OR operations
 - ❑ $C=1$, to implement OR and $C=0$, to implement AND operation
- ❑ Important: TRA destroys contents of the involved cells
 - ❑ Contents need to be copied to a different place first, if important/needed

Ambit -- CIM-logic using DRAM

 


- ❑ Dedicated compute rows (B-group) to simplify the row-decoder design

Ambit -- CIM-logic using DRAM

 

- ❑ Dedicated compute rows (B-group) to simplify the row-decoder design
- ❑ The two control/constants rows (C-group) have constant 0 (C0) and 1 (C1)

Ambit -- CIM-logic using DRAM

 

- ❑ Dedicated compute rows (B-group) to simplify the row-decoder design
- ❑ The two control/constants rows (C-group) have constant 0 (C0) and 1 (C1)
- ❑ Majority of the rows are data rows (D-group), as in a typical DRAM array

Ambit -- CIM-logic using DRAM

- ❑ To perform a logic AND using Ambit:
 1. Copy A to T0
 2. Copy B to T1
 3. Copy C0 to T2
 4. Activate T0, T1, and T2 simultaneously
 5. Copy T0 to R (resultant row)

Ambit -- CIM-logic using DRAM

❑ To perform a logic AND using Ambit:

1. Copy A to T0
2. Copy B to T1
3. Copy C0 to T2
4. Activate T0, T1, and T2 simultaneously
5. Copy T0 to R (resultant row)

❑ For logical OR, copy C1 in step 3 instead of C0

Ambit -- CIM-logic using DRAM

- ❑ To perform a logic AND using Ambit:
 1. Copy A to T0
 2. Copy B to T1
 3. Copy C0 to T2
 4. Activate T0, T1, and T2 simultaneously
 5. Copy T0 to R (resultant row)
- ❑ For logical OR, copy C1 in step 3 instead of C0
- ❑ Now that you know all the needed steps, how would you perform D_i & D_j , using AAP commands ?

Ambit -- CIM-logic using DRAM

❑ To perform a logic AND using Ambit:

1. Copy A to T0
2. Copy B to T1
3. Copy C0 to T2
4. Activate T0, T1, and T2 simultaneously
5. Copy T0 to R (resultant row)

```
AAP (Di, B0) ;T0 = Di
AAP (Dj, B1) ;T1 = Dj
AAP (C0, B2) ;T2 = 0
AAP (B12, Dk) ;Dk = T0 & T1
```

❑ For logical OR, copy C1 in step 3 instead of C0

❑ Now that you know all the needed steps, how would you perform D_i & D_j , using AAP commands ?

Ambit -- CIM-logic using DRAM

❑ To perform a logic AND using Ambit:

1. Copy A to T0
2. Copy B to T1
3. Copy C0 to T2
4. Activate T0, T1, and T2 simultaneously
5. Copy T0 to R (resultant row)


```
AAP (Di, B0) ;T0 = Di
AAP (Dj, B1) ;T1 = Dj
AAP (C0, B2) ;T2 = 0
AAP (B12, Dk) ;Dk = T0 & T1
```

❑ For logical OR, copy C1 in step 3 instead of C0

❑ Now that you know all the needed steps, how would you perform D_i & D_j , using AAP commands ?

❑ The NOT operation is implemented using inverted bitline, and specialized DRAM cells


In-DRAM addition

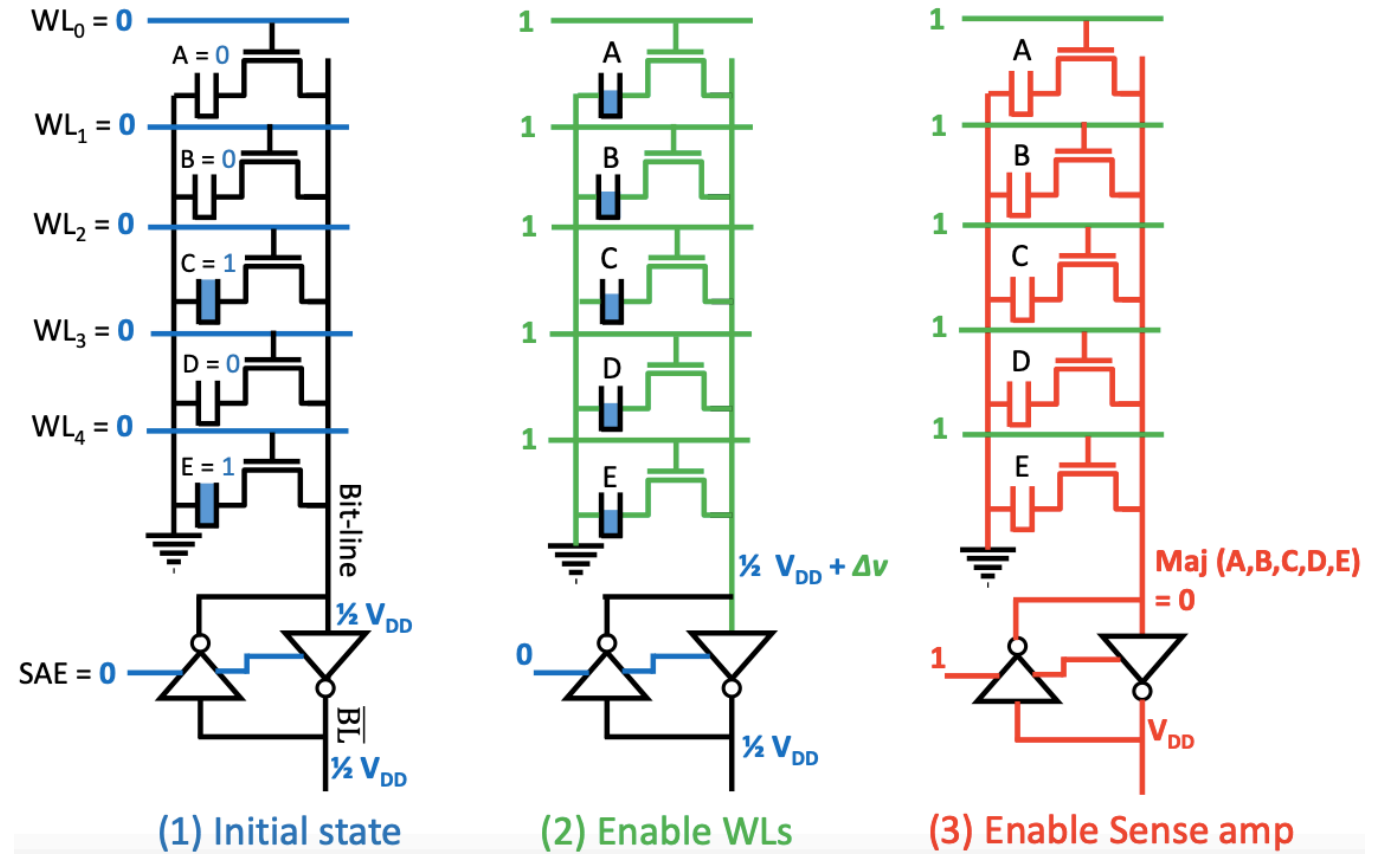

In-DRAM addition

$$C_{out} = Majority(A, B, C_{in})$$
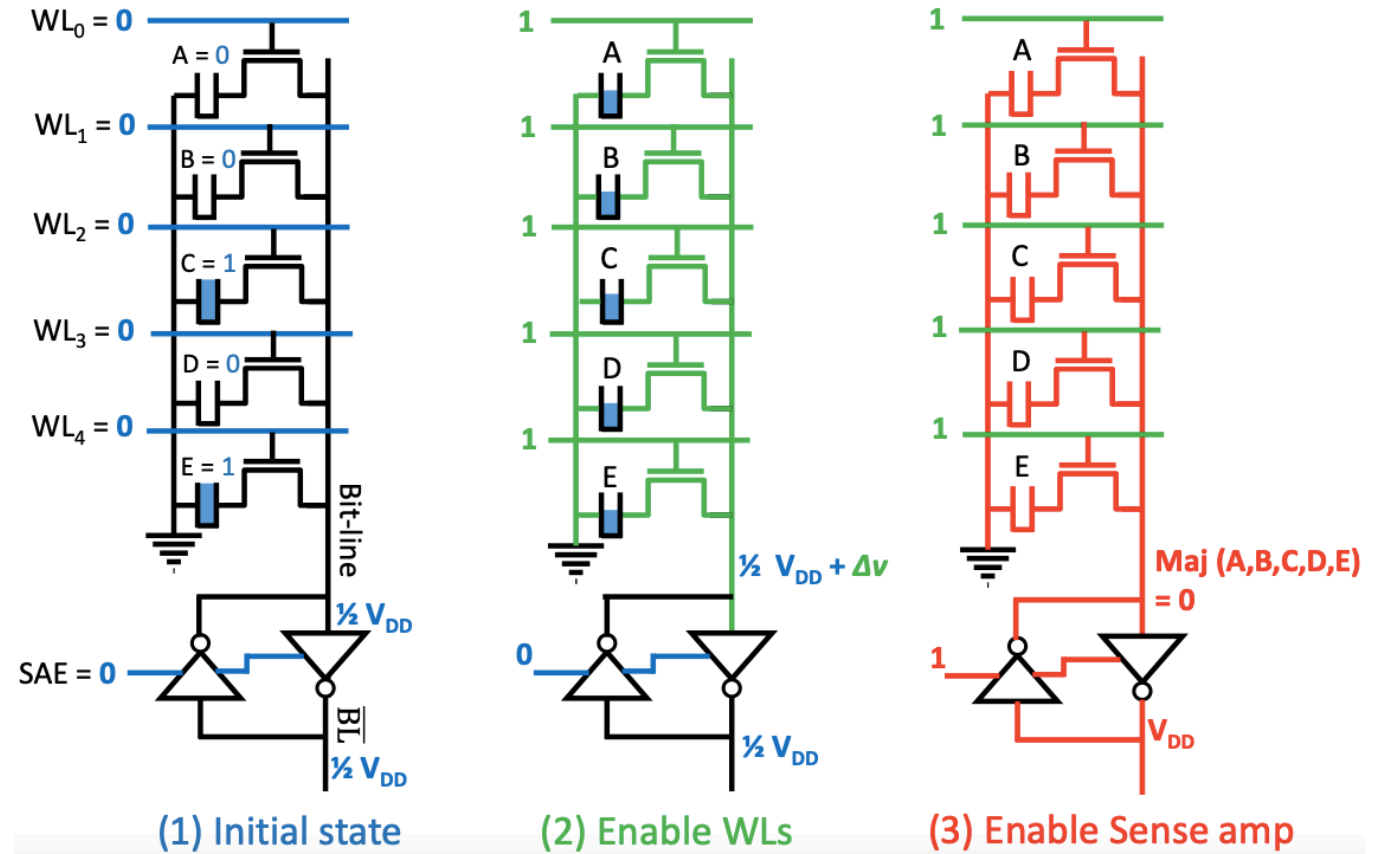
$$Sum = Majority(A, B, C_{in}, \overline{C_{out}}, \overline{C_{out}})$$




In-DRAM addition

$$C_{out} = Majority(A, B, C_{in})$$

$$Sum = Majority(A, B, C_{in}, \overline{C_{out}}, \overline{C_{out}})$$

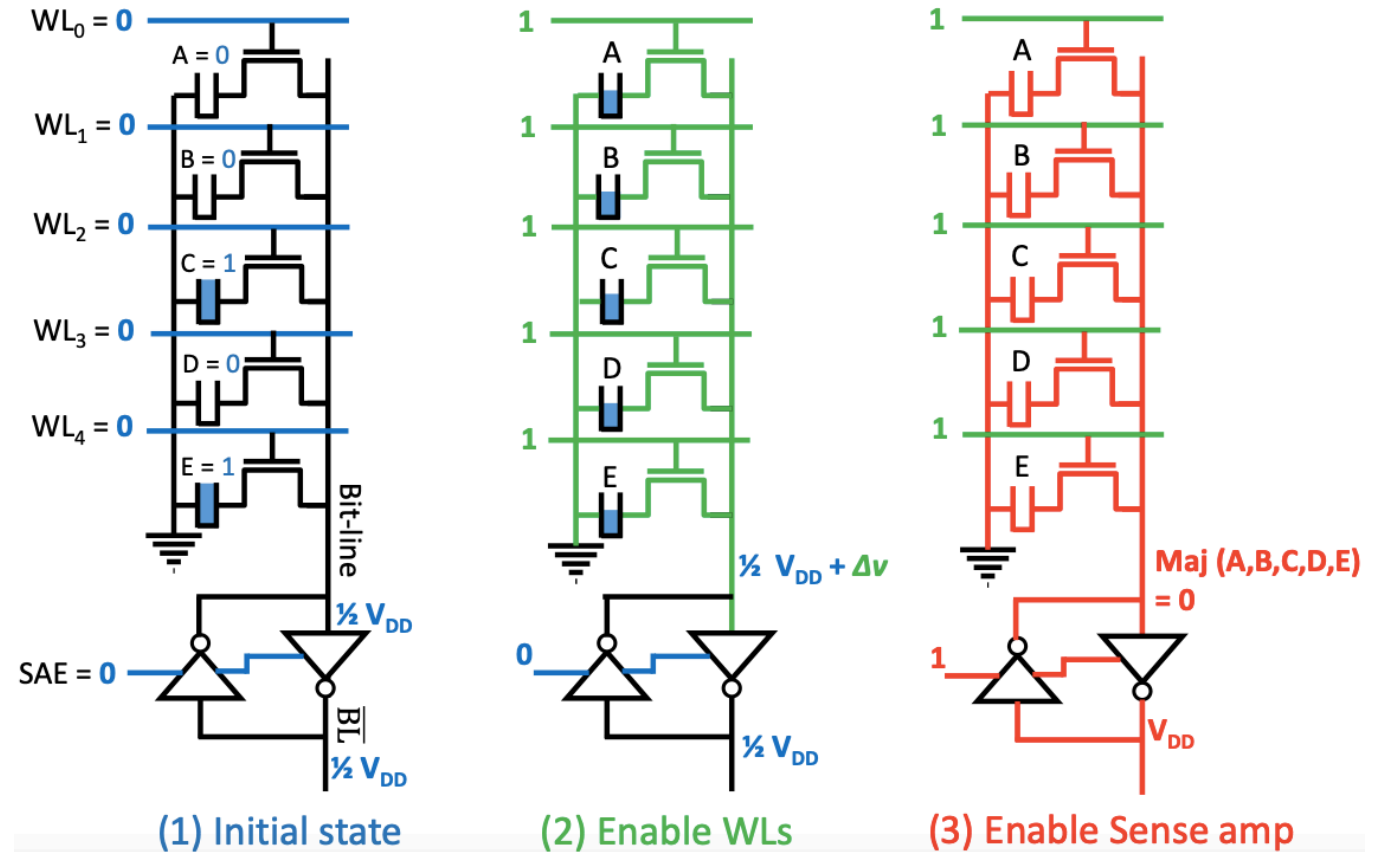- Note that the operations are bit-serial




In-DRAM addition

$$C_{out} = \text{Majority}(A, B, C_{in})$$

$$Sum = \text{Majority}(A, B, C_{in}, \overline{C_{out}}, \overline{C_{out}})$$

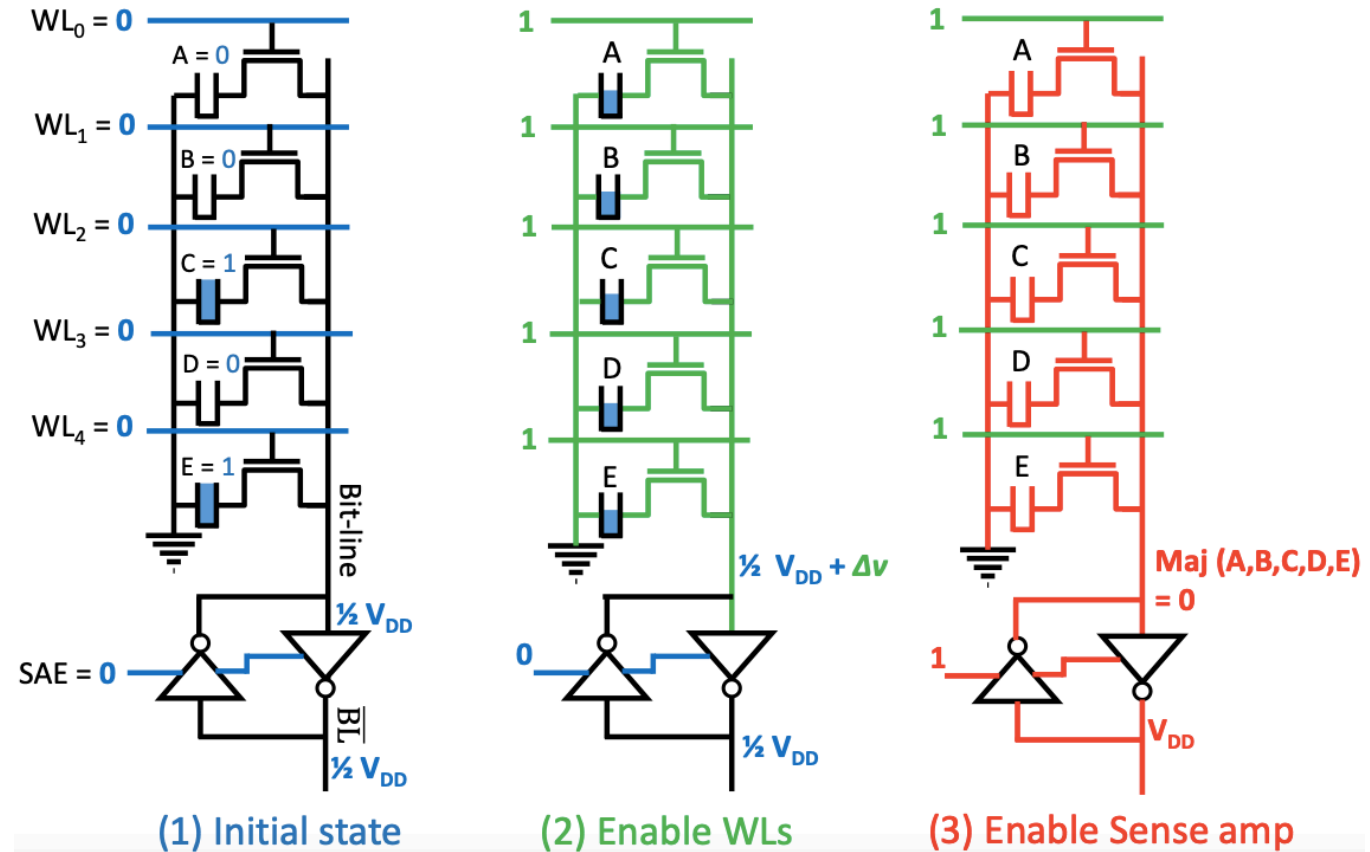- Note that the operations are bit-serial
- ... but word-parallel




In-DRAM addition

$$C_{out} = \text{Majority}(A, B, C_{in})$$

$$Sum = \text{Majority}(A, B, C_{in}, \overline{C_{out}}, \overline{C_{out}})$$

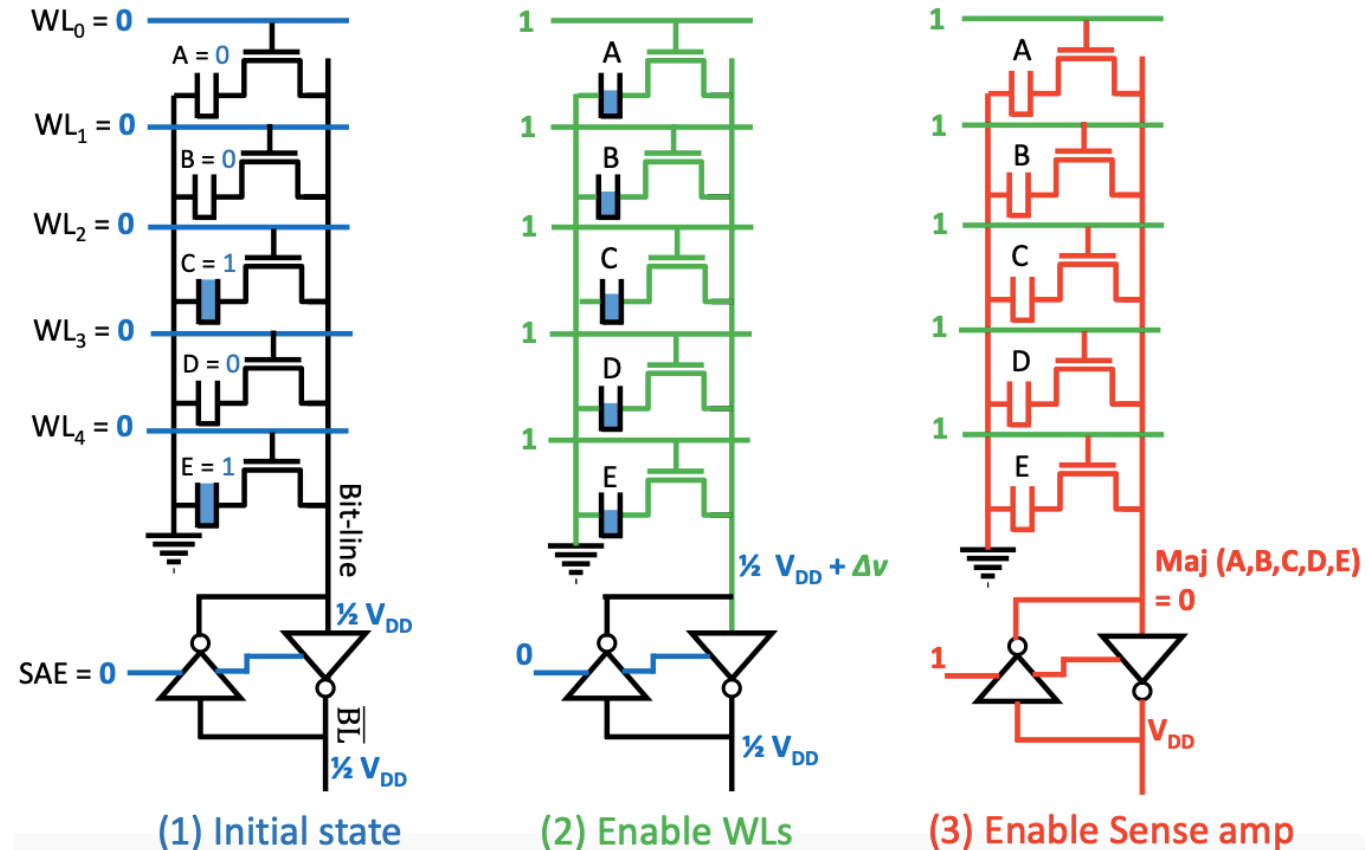- ❑ Note that the operations are bit-serial
- ❑ ... but word-parallel
- ❑ Particularly useful for bulk additions on low-precision numbers



Other operations using CIM-DRAM

- ❑ *Majority* can also be used to implement other operations (logic, arithmetic)

Other operations using CIM-DRAM

- ❑ *Majority* can also be used to implement other operations (logic, arithmetic)
- ❑ For masked counting using DRAM:
 - ❑ Assuming Johnson encoding
 - ❑ The shifting and invert-back can be implemented using basic in-DRAM ops.

Other operations using CIM-DRAM

- ❑ *Majority* can also be used to implement other operations (logic, arithmetic)
- ❑ For masked counting using DRAM:
 - ❑ Assuming Johnson encoding
 - ❑ The shifting and invert-back can be implemented using basic in-DRAM ops.

$$b_i = (b_i \wedge \overline{m}) \vee (b_{i-1} \wedge m), \quad \text{where } i \in \{n, n-1, \dots, 2\}$$

$$b_1 = (b_1 \wedge \overline{m}) \vee (\overline{b_n} \wedge m)$$

CIM-logic using memristors


- ❑ The fundamental idea is similar to DRAM, i.e., multi-row activation

CIM-logic using memristors

- ❑ The fundamental idea is similar to DRAM, i.e., multi-row activation
- ❑ The output is compared to a reference voltage

CIM-logic using memristors

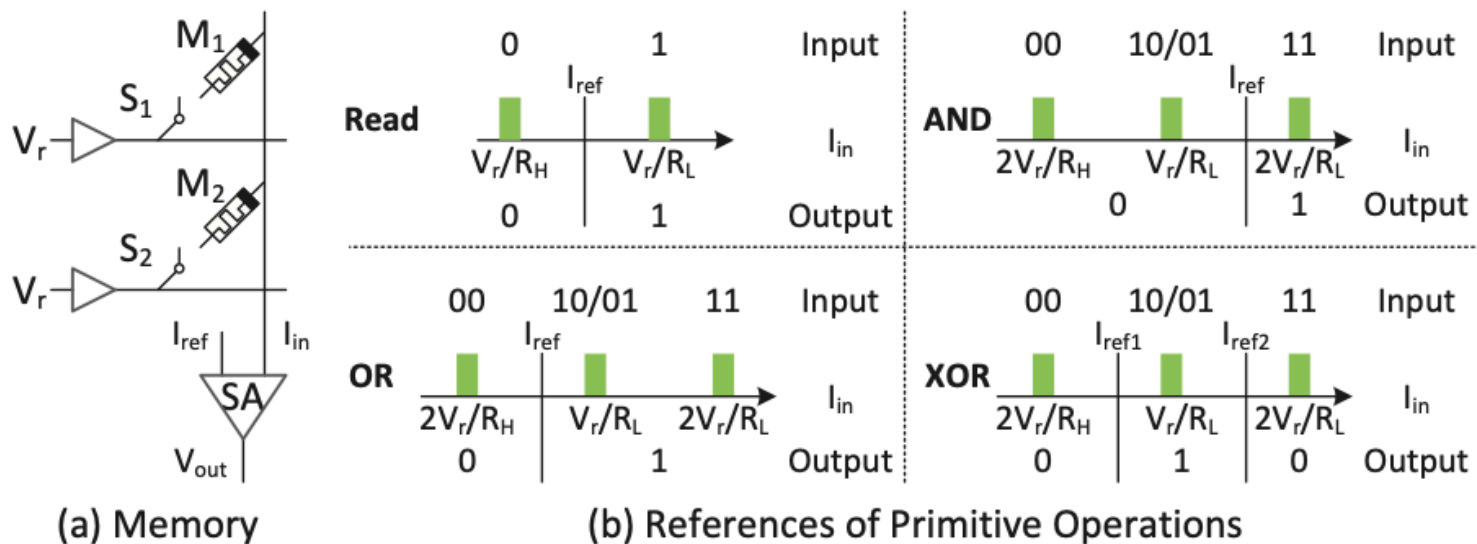- ❑ The fundamental idea is similar to DRAM, i.e., multi-row activation
- ❑ The output is compared to a reference voltage



Thank you!
asif.ali@uetpeshawar.edu.pk