



Department of Computer Systems Engineering
University of Engineering & Technology
Peshawar, PAKISTAN

Subject: Signal and Systems (4th Semester)

Exam: Final Term (Spring 2018)

Max Marks: 25, Time allowed: 2 hours

Question 1:

- 1) For the continuous-time periodic signal $x(t)$ given below; (CLO 3) (4 Marks)

$$x(t) = 3 + \cos\left(\frac{\pi}{6}t + \frac{\pi}{6}\right) + 2\sin\left(\frac{\pi}{2}t + \frac{\pi}{2}\right) + 2\sin\left(\frac{2\pi}{3}t + \frac{\pi}{4}\right)$$

Find the fundamental frequency ω_0 and Fourier series coefficients a_k , also draw the spectrum of the signal $x(t)$.

- 2) Find the output $y(t)$ when the signal $x(t)$ given in part (1) above is passed through an LTI system with impulse response $h(t)$ given below. (CLO 4) (3 Marks)

$$h(t) = e^{-2t}u(t)$$

Question 2:

- 1) Find the Fourier series coefficients of the periodic discrete-time signal $x[n]$ shown in Figure 1. Also draw its magnitude and phase spectrum. (CLO 3) (2+2 Marks)

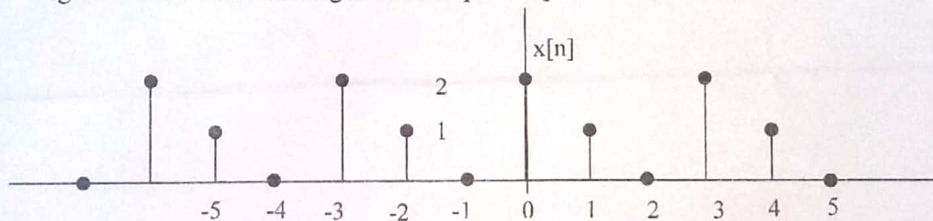


Figure 1

- 2) If the Fourier Series coefficients of a discrete-time periodic signal $x[n]$ are denoted by a_k , find the coefficients for the signal $x_1[n]$ given below in terms of a_k .

$$x_1[n] = x[n] - x[n-1]$$

Using the above concept find the spectrum of signal $x_2[n] = x[n-1]$. Draw the magnitude and phase spectrum of $x_2[n]$ and compare it with spectrum obtained in part(a) above. (CLO 3) (2+1+1+1 Marks)

Question 3:

- 1) Use Fourier transform to find the convolution of $x(t)$ and $h(t)$ given below. (CLO 4) (3)

$$x(t) = e^{-2t}u(t)$$

$$h(t) = e^{-3t}u(t)$$

- 2) Use Fourier Transform method to find the impulse response of the LTI system given by the following difference equation. (CLO4) (3+3 Marks)

$$y[n] + \frac{1}{2}y[n-1] = x[n]$$

Also find the response of this system to the input signal $x[n]$ given below;

$$x[n] = \left(\frac{1}{4}\right)^n u[n]$$


Electronic Circuits
Semester 4
Spring 2018 Final Exam

Q1


(Marks: 7+8)

- Draw the connection diagram of a **common emitter (CE)** PNP transistor configuration showing the transistor symbol, biasing voltage sources and current flow directions.
- Draw the input and output voltage-current characteristic curves for a **common base (CB)** BJT configuration using proper subscripts for V and I. Tag the different regions in the graph.

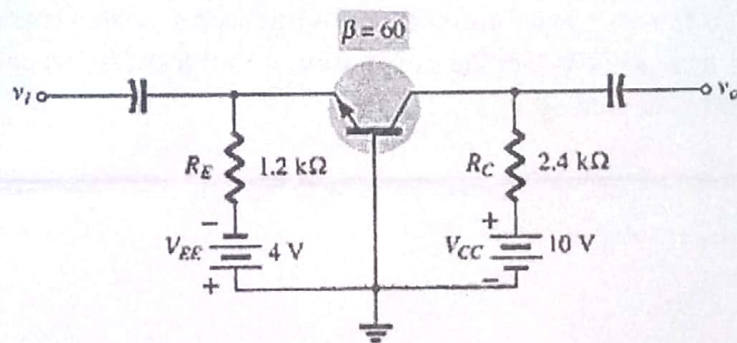Q2 Determine the currents I_E and I_B and the voltages V_{CE} and V_{CB} for the common-base configuration of the following figure. (Marks:15)



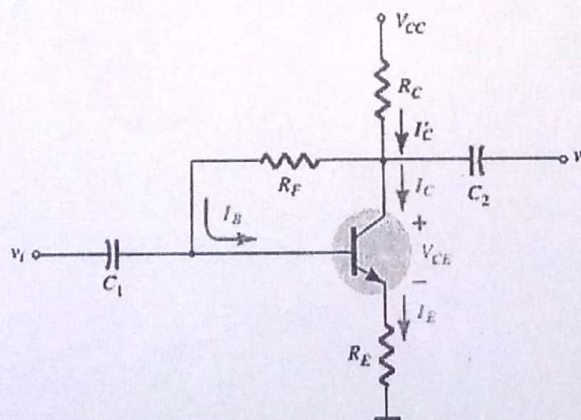Q3 For the Collector Feedback configuration of the following figure, derive an expression for current I_B . (Marks:10)



✓ Q4

(Marks:10+10)

- a) Draw the AC-equivalent circuit for a Common Emitter (CE), Emitter-biased configuration (unbypassed) using r_e transistor model.
- b) Derive expressions for the input impedance Z_i , output impedance Z_o and voltage gain A_v for the above stated network.

✓ Q5 Draw the symbols for the following devices:

(Marks: 2+2+2+2+2)

- a) PNP transistor
- b) P-channel JFET
- c) N-channel Depletion type MOSFET
- d) P-channel Enhancement type MOSFET
- e) N-channel Enhancement type MOSFET

✓ Q6 Draw the drain and transfer characteristic curves for an n-channel JFET with $I_{DSS} = 12$ mA and $V_p = -6$ V. Plot the curves using at least four (V_{GS} , I_D) points derived with shorthand method.

(Marks:15)

✓ Q7 Design a digital inverter circuit using Complementary MOSFETS and show how it satisfies the truth table.

(Marks: 15)

END

OF SEMESTER